

Instructions

The question paper consists of multiple-choice questions, with each question carrying 4 marks. The question paper contains 80 questions, 20 questions from Physics and 60 questions from Biology.

Each correct answer will be awarded 4 marks, while 1 mark will be deducted for each incorrect answer. Candidates must carefully fill out the OMR Sheet with a black or blue ballpoint pen. Once an answer is marked on the OMR sheet, it cannot be erased or modified. Question marked with more than one options will be treated as wrong.

- 1. Kirchhoff's Junction Rule is based on the law of conservation of:
 - A) Energy
 - B) Momentum
 - C) Charge
 - D) Mass
- 2. According to Kirchhoff's Loop Rule, the algebraic sum of potential differences in a closed loop is:
 - A) $I V$
 - B) Zero
 - C) Infinite
 - D) Equal to emf

- 3. In a junction, 5 A current enters and 2 A and 1 A leave. The third outgoing current is:
 - A) 1 A
 - B) 2 A
 - C) 3 A
 - D) 4 A

The unit of Joule's heating is: A) Volt
 B) Ampere
 C) Joule
 D) Ohm

D) $I^2 R t$

- 6. A 10Ω resistor carries 2 A current for 5 s. Heat produced is:
 - A) 100 J
 - B) 200 J
 - C) 50 J
 - D) 25 J

- 7. In a Wheatstone bridge, the bridge is balanced when:
 - A) $P + Q = R + S$
 - B) $P/Q = R/S$
 - C) $P \times Q = R \times S$
 - D) $P = Q = R = S$

- 8. In a balanced Wheatstone bridge, the current through galvanometer is:
 - A) Maximum
 - B) Minimum
 - C) Zero
 - D) Infinite


- 9. The Wheatstone bridge is used to measure:
 - A) Voltage
 - B) Current
 - C) Resistance
 - D) Power

TIME = 1.5


MONDAY TEST - Electricity + Capacitance
 CLASS - XII
 SUBJECT - Physics

Q1. A capacitor of capacitance C is charged to a potential V . The flux of the electric field through a closed surface enclosing the positive plate of the capacitor is: (a) $\frac{CV}{\epsilon_0}$ (b) $\frac{2CV}{\epsilon_0}$ (c) $\frac{CV}{\epsilon_0}$ (d) zero.

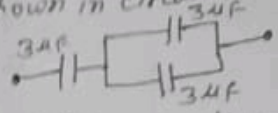Q2. The equivalent capacitance of the system shown in circuit is:
 (a) $3 \mu F$ (b) $6 \mu F$ (c) $9 \mu F$ (d) $2 \mu F$.



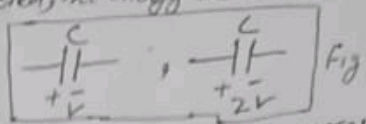
Q3. Two capacitors are charged as shown in fig. When both the +ve terminals of capacitors are connected, the energy loss will be
 (a) $\frac{1}{2} CV^2$ (b) $\frac{3}{4} CV^2$ (c) $\frac{1}{4} CV^2$ (d) $2 CV^2$



Q4. Two metal wires of identical dimensions are connected in series. If σ_1 and σ_2 are the conductivities of the metal wires respectively, the effective conductivity of the combination is (a) $\frac{\sigma_1 \sigma_2}{\sigma_1 + \sigma_2}$ (b) $\frac{\sigma_1 + \sigma_2}{2 \sigma_1 \sigma_2}$


(c) $\frac{2 \sigma_1 \sigma_2}{\sigma_1 + \sigma_2}$ (d) $\frac{\sigma_1 + \sigma_2}{\sigma_1 \sigma_2}$

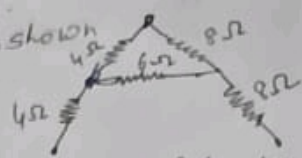Q5. The equivalent resistance between A and B for the mesh shown is
 (a) 4.8Ω (b) 7.2Ω (c) 16Ω (d) 30Ω



SECTION-B $2 \times 4 = 8$

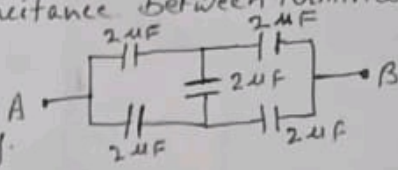Q6. In the circuit, find the equivalent capacitance between terminal A and B. Also calculate it.
 (a) $2 \mu F$ (b) $1 \mu F$ (c) $0.5 \mu F$ (d) $4 \mu F$



Q7. Derive the expression for the capacitance of a parallel plate capacitor.


Q8. Deduce the Ohm's law from the concept of drift velocity.

Q9. State Kirchhoff's Rule using sign convention explain II rule. Why current is a scalar quantity.

SECTION-C $3 \times 4 = 12$

Q10. Find the value of the unknown resistance X , in the following circuit, if no current flows through the section AO , as shown in diagram calculate the current drawn by circuit from the battery of emf $6V$ and negligible internal resistance.

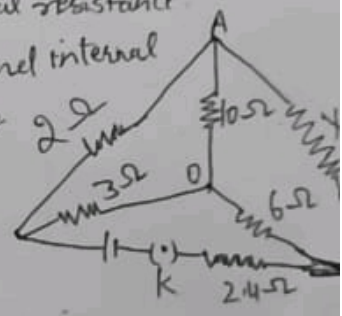Q11. Derive the expression for the equivalent emf and internal resistance of the combination of cell of emf ϵ_1 and ϵ_2 in parallel.



Q13. Using Kirchhoff's Rule, verify and state Wheatstone Bridge.

Q14. Using Kirchhoff's Rule, write/calculate the current i_1 and i_2 in the circuit. Diagram as shown below.