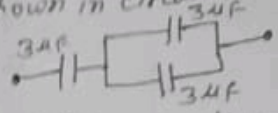


TIME = 1.5


MONDAY TEST - Electricity + Capacitance
 CLASS - XII
 SUBJECT - Physics

Q1. A capacitor of capacitance C is charged to a potential V . The flux of the electric field through a closed surface enclosing the positive plate of the capacitor is: (a) $\frac{CV}{\epsilon_0}$ (b) $\frac{2CV}{\epsilon_0}$ (c) $\frac{CV}{\epsilon_0}$ (d) zero.

Q2. The equivalent capacitance of the system shown in circuit is:
 (a) $3 \mu F$ (b) $6 \mu F$ (c) $9 \mu F$ (d) $2 \mu F$.



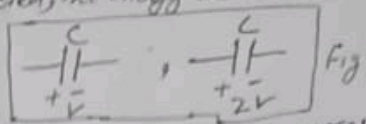
Q3. Two capacitors are charged as shown in Fig. When both the +ve terminals of capacitors are connected, the energy loss will be
 (a) $\frac{1}{2} CV^2$ (b) $\frac{3}{4} CV^2$ (c) $\frac{1}{4} CV^2$ (d) $2 CV^2$



Q4. Two metal wires of identical dimensions are connected in series. If σ_1 and σ_2 are the conductivities of the metal wires respectively, the effective conductivity of the combination is (a) $\frac{\sigma_1 \sigma_2}{\sigma_1 + \sigma_2}$ (b) $\frac{\sigma_1 + \sigma_2}{2 \sigma_1 \sigma_2}$


(c) $\frac{2 \sigma_1 \sigma_2}{\sigma_1 + \sigma_2}$ (d) $\frac{\sigma_1 + \sigma_2}{\sigma_1 \sigma_2}$

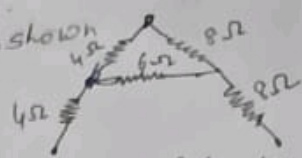Q5. The equivalent resistance between A and B for the mesh shown is
 (a) 4.8Ω (b) 7.2Ω (c) 16Ω (d) 30Ω



SECTION-B $2 \times 4 = 8$

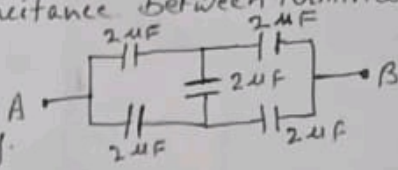Q6. In the circuit, find the equivalent capacitance between terminal A and B. Also calculate it.
 (a) $2 \mu F$ (b) $1 \mu F$ (c) $0.5 \mu F$ (d) $4 \mu F$



Q7. Derive the expression for the capacitance of a parallel plate capacitor.


Q8. Deduce the Ohm's law from the concept of drift velocity.

Q9. State Kirchhoff's Rule using sign convention explain II rule. Why current is a scalar quantity.

SECTION-C $3 \times 4 = 12$

Q10. Find the value of the unknown resistance X , in the following circuit, if no current flows through the section AO , as shown in diagram calculate the current drawn by circuit from the battery of emf $6V$ and negligible internal resistance.

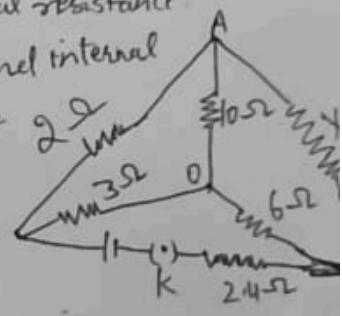Q11. Derive the expression for the equivalent emf and internal resistance of the combination of cell of emf \mathcal{E}_1 and \mathcal{E}_2 in parallel.



Q13. Using Kirchhoff's Rule, verify and state Wheatstone Bridge.

Q14. Using Kirchhoff's Rule, write/calculate the current i_1 and i_2 in the circuit. Diagram as shown below.