




Suggested Remedial Action:

Ask students to give the reason for their answer. Take two and put them on a table. Ask students a similar question glasses from their place. They may say that they are made of glass. Check what the glasses are made up of by touching them. They may say that they are made of glass. Check them again if they can observe option 2 just by looking at the answer. Making observations is the first step in any cases where they observe things and note them down.

3

Q Shown here is a circuit made by Ashwin.

31

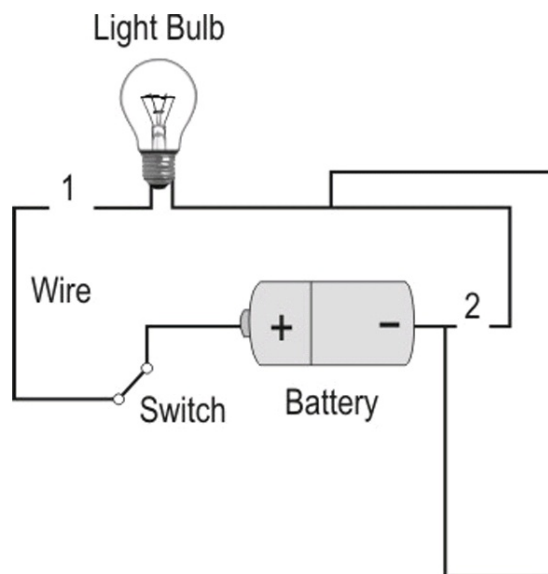

Which of the following change(s) in the circuit i bulb glow?

- i. connecting a wire to both ends at point 1.**
- ii. connecting a wire to both ends at point 2.**
- iii. reversing the battery**

- 1** only i
- 2** only iii
- 3** both i and ii
- 4** (No change is needed; the bulb will glow in the g



Edit PDF



Comment



Highlight



Draw



Fill & Sign



More tools